



Sabratha University
Engineering Faculty Sabratha
EEE-Department

Summing Operational Amplifier

Author: Nedal Abdullah

ID: 1611100336

1. Objectives

The objective of this experiment is to study and simulating summing configuration of 741 operational-amplifier using multisim simulating kit.

2. Equipment

- a. Oscilloscope
- b. Multimeter
- c. AC Source
- d. Switches
- e. Vcc (+15v)
- f. Vdd (-15v)
- g. IC-741
- h. Resistors(1k Ω , 2k Ω , 3k Ω , 4k Ω)

3. Circuit Diagram

Figure 1 shows the circuit diagram for two input summing configuration.


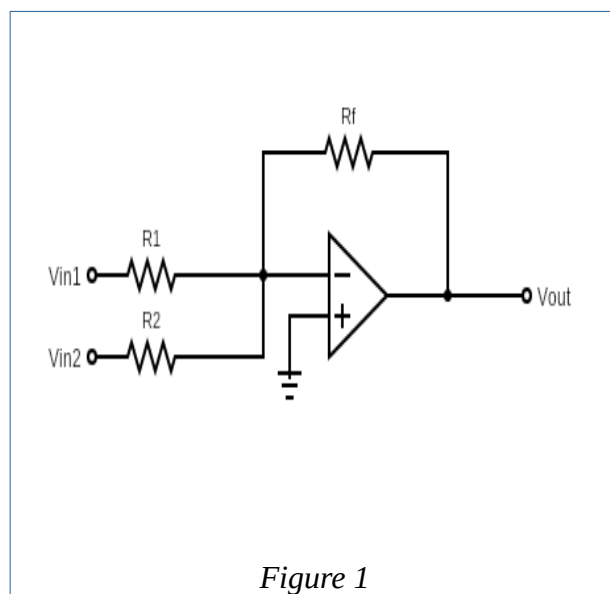


Figure 2 shows the circuit connection for two input summing configuration on multisim simulating application.

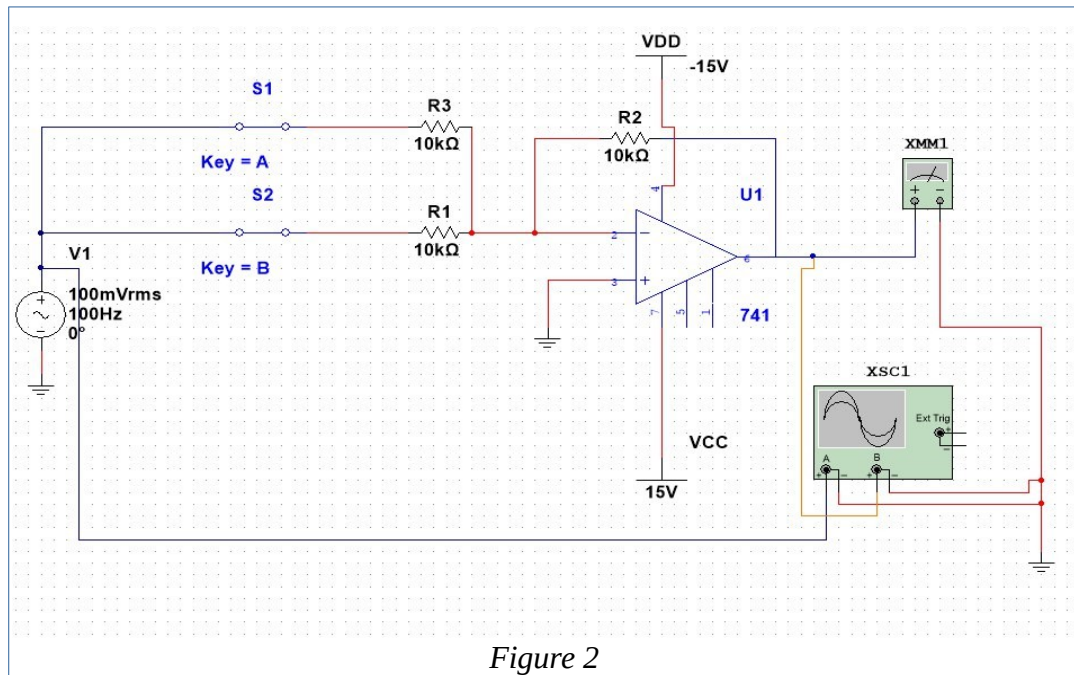

4. Theory

A modern op-amp has hundreds of transistors integrated on a single chip, It is not necessary to understand how the internal circuitry works in order to use the op-amp; it can be treated as a “black-box” device.

The symbol for an 741 op-amp is shown in figure 1, This is the most basic op-amp symbol with five terminals comprised of positive (non-inverting) and negative (inverting) inputs; V+ and V- supply terminals; and one output.

All equations that describe the behavior of op-amp circuits rely on certain assumptions about the op-amp. These assumptions about an ideal op-amp are summarized in table 1 and compared to the real op-amp used in this lab, the 741.

A modern op-amp approaches an ideal op-amp when used within its bandwidth and output limitations. For non-critical applications the ideal op-amp assumptions are valid.

In the case of the 741 as long as the device is operated at low frequencies and does not exceed its rated output voltage and current limits the ideal assumptions are valid.

Parameter	Ideal Op-Amp	741
R_{in}	Infinite	$2M\Omega$
Open loop Gain	Infinite	200,000
Bandwidth	Infinite	1MHz
Voltage Output	Infinite	+/- 15.0V
Current Output	Infinite	25mA
R_o	Zero	75Ω
Input Offset Voltage	Zero	1mV
Input Bias Current	Zero	0.2nA

Table 1

The behavior of an op-amp can be described by two rules:

1. An op-amp will attempt to make the voltage at both its inputs equal through the use of a feedback path.

2. No current can flow through inputs terminals.

Now by connected the 741 as shown in figure 1, we will get the summing operation amplifier configuration and this configuration has a negative gain and negative feedback loop and this configuration can add two input voltage together and for this configuration the input/output relationship is given by:

$$V_o = -\left(\frac{R_f}{R_{in}} V_1 + \frac{R_f}{R_{in}} V_2\right)$$

Formula 1

in case of R_f equal R_{in} the output will given by the Formula 2:

$$V_o = -(V_1 + V_2)$$

Formula 2

5. Observation Data

● Simulation Readings

Table 2 shows all the readings that we got from the simulation using different values of R_2 and different input voltages.

$V_1(\text{v})$	$V_2(\text{v})$	$R_1(\text{k}\Omega)$	$R_3(\text{k}\Omega)$	$R_2(\text{k}\Omega)$	$V_{\text{o-real}}(\text{v})$	$V_{\text{o-sim}}(\text{v})$	$F(\text{Hz})$	Error(%)
0.1	0.1	10	10	10	-0.2	-0.1999	1000	0.005
0.5	0.5	10	10	10	-1	-0.9999	1000	0.003
1	1	10	10	10	-2	-2	1000	0
2	2	10	10	10	-4	-4	1000	0
5	5	10	10	10	-10	-9.9999	1000	0.010
10	10	10	10	10	-20(cut)	-12.493	1000	37.535
0.1	0.1	10	10	100	-2	-1.999	1000	0.005
0.5	0.5	10	10	100	-10	-9.9960	1000	0.040

Table 2

Table 3 shows the Frequency Response for the 741 operational amplifier.

$V_1(\text{v})$	$V_2(\text{v})$	$R_1(\text{k}\Omega)$	$R_3(\text{k}\Omega)$	$R_2(\text{k}\Omega)$	$F(\text{Hz})$	$V_{\text{o-real}}(\text{v})$
0.5	0.5	10	10	10	10	1.0010
0.5	0.5	10	10	10	100	0.9999
0.5	0.5	10	10	10	100	0.9999
0.5	0.5	10	10	10	100k	0.6957
0.5	0.5	10	10	10	1M	0.0710
0.5	0.5	10	10	10	10M	0.0077

Table 3

- Oscilloscope output

The Figure 3 shows the input signal and the summing output signal on the Oscilloscope.


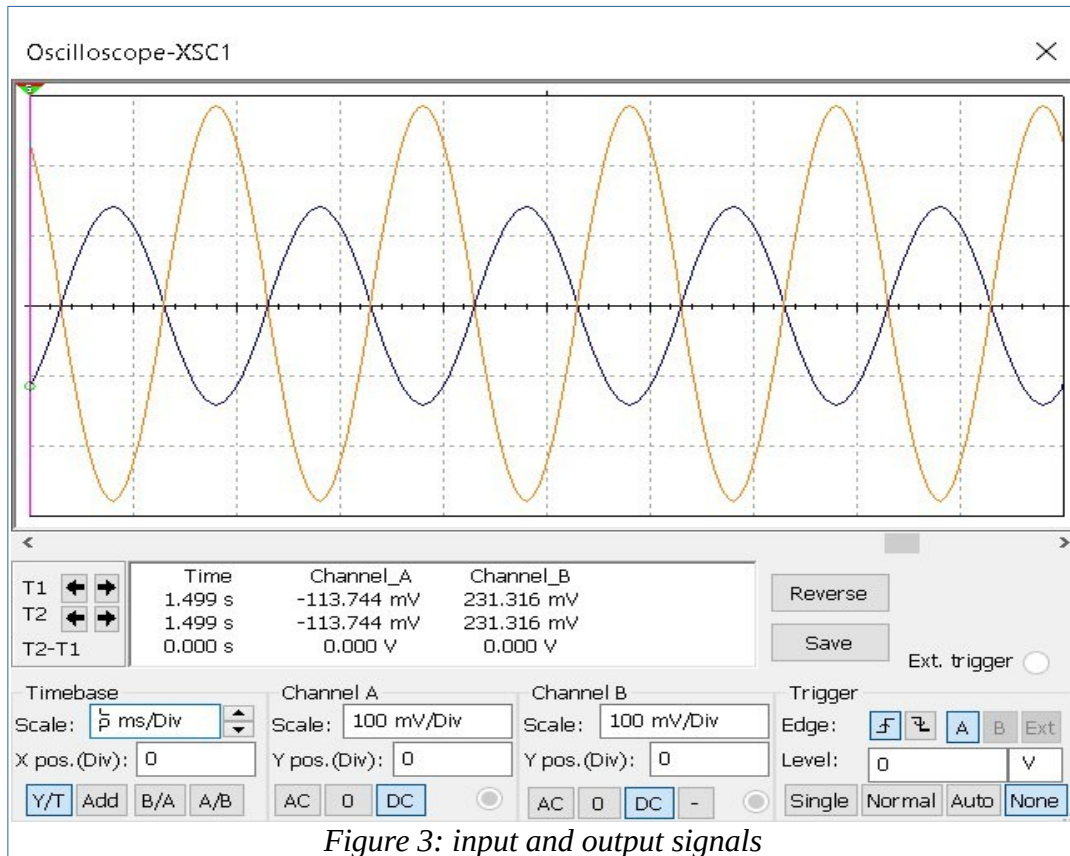


Figure 3: input and output signals

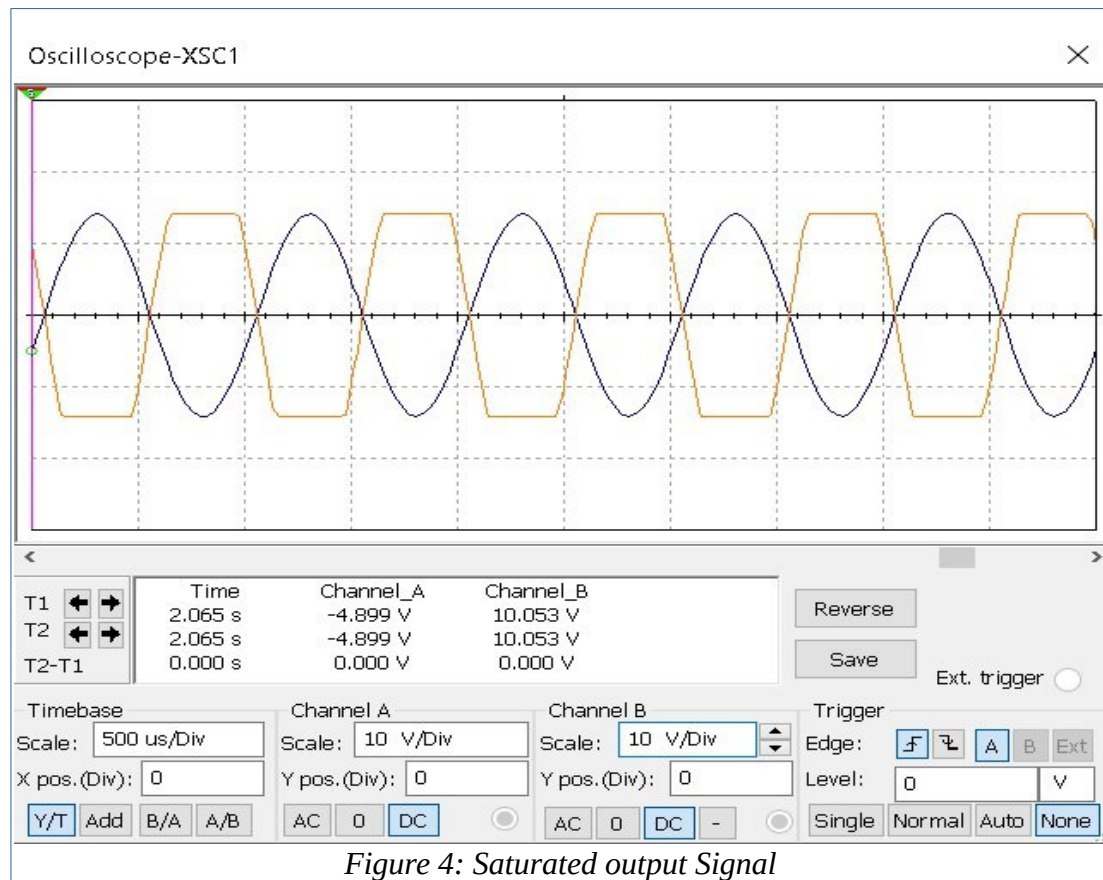The Figure 4 shows the input signal and Saturated Output signal.



The Figure 5 shows the input signal and zero Output signal when both switches are open

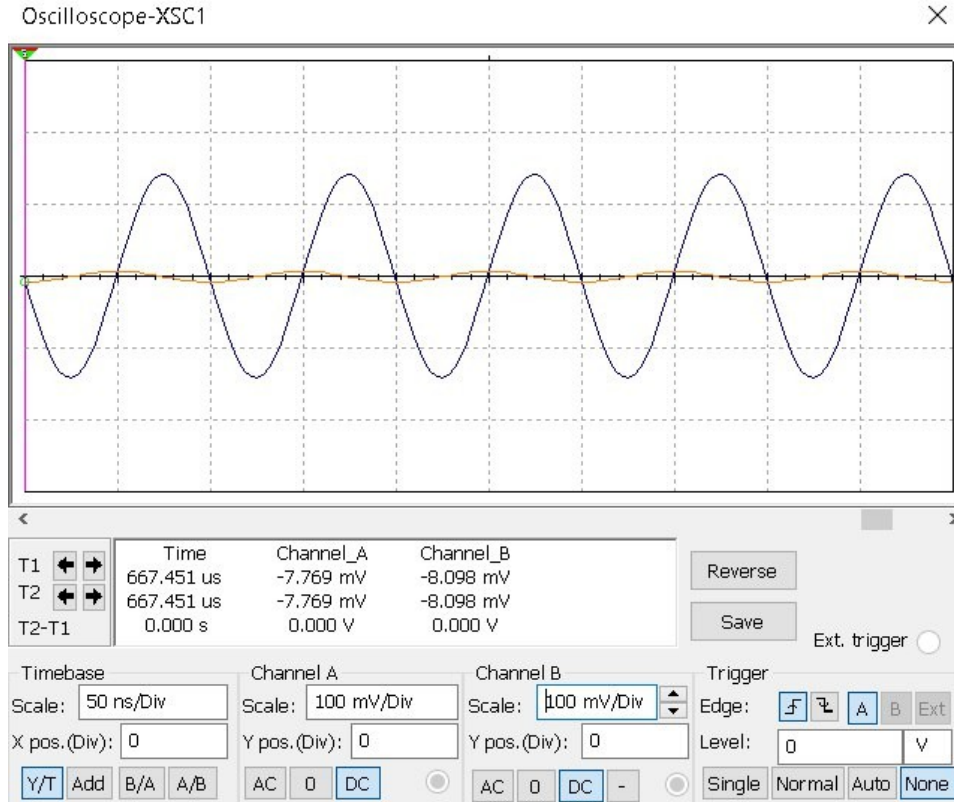


Figure 5: Both Switches are Opened

- **Multimeter output**

The Figure 6 shows the Output signal Voltage value when both switches are closed

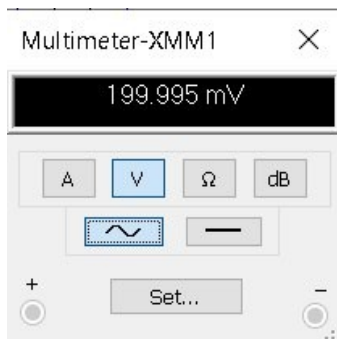


Figure 6: Both Switches are Closed

The Figure 7 shows the Output signal Voltage value when both switches are opened

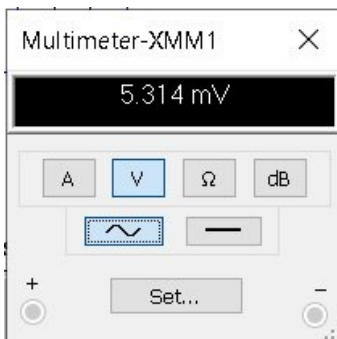


Figure 7: Both Switches are Opened

6. Graphs

The Figure 8 shows the graph between Theoretical Output and Actual Output.

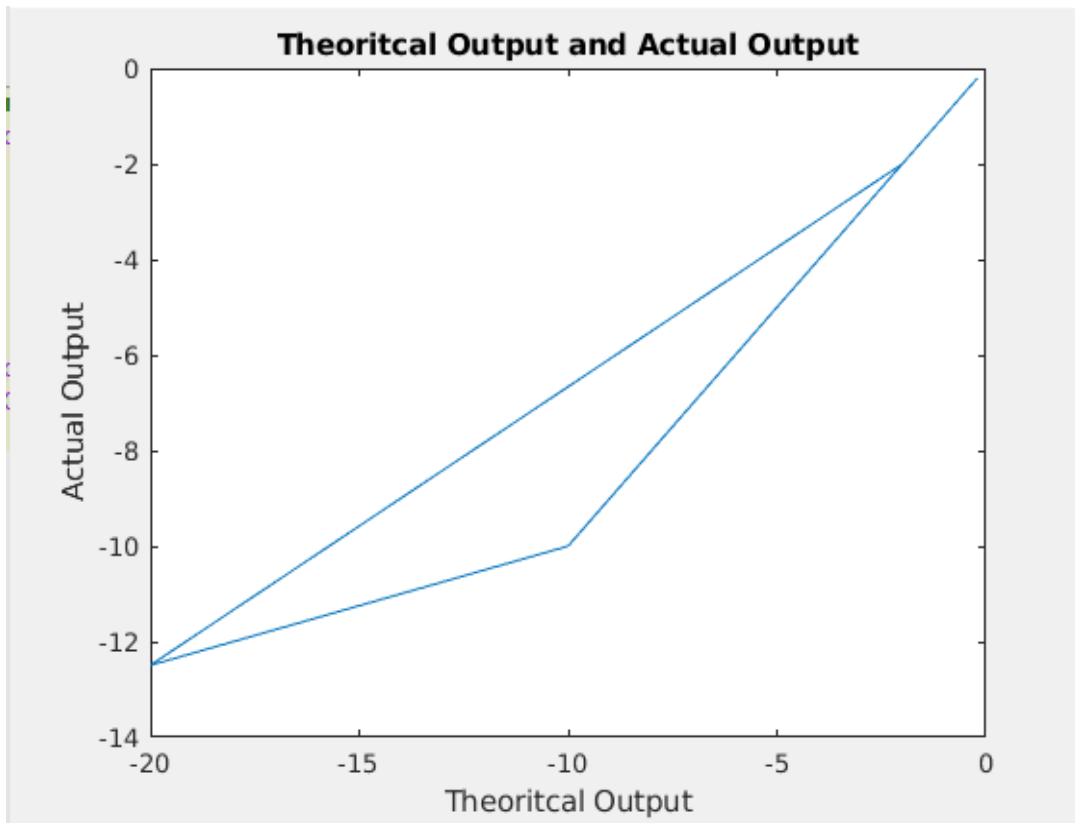


Figure 8: Theoretical Output and Actual Output

The Figure 9 shows the Frequency Response for 741 op-amp in summing configuration

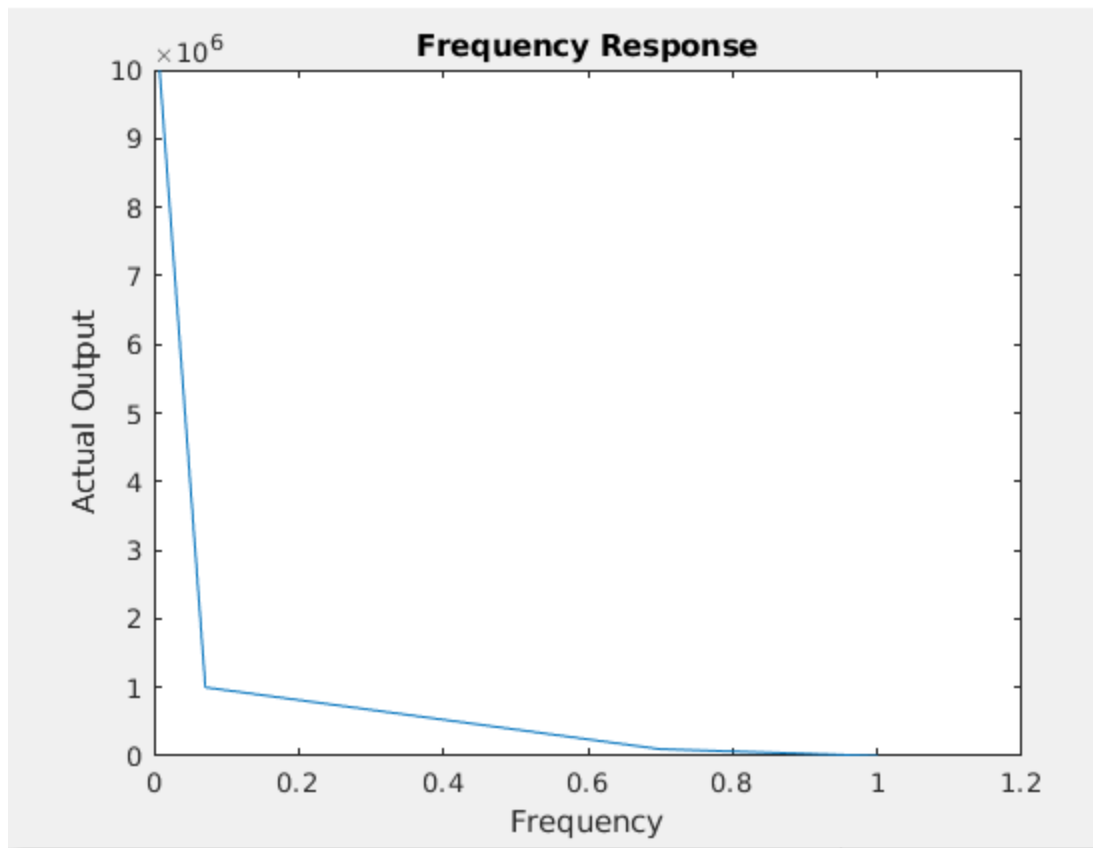


Figure 9: Frequency Response

7. Analysis

From the readings that we got from simulating and showed in Table 2 we can see that the output depend on input and we can change the Gain by changing the Value R_2 and we can see that we can't get the Theoretical output voltage because there is an Output Resistance For operational amplifier and its value shown in Table 1.

If we see the Figure 4 we can notice that we got a cutting on output signal and that happened because the Amplified signal is Limited to the supply inputs voltages (+Vcc / -Vdd) and we can avoid that by increasing the input voltages but notice that

we got a maximum value of input voltages for IC-741 as shown in Table 1, and from the Figure 3 we can see that output signal is the two input signals added together and the output is out-phase (negative-gain).

8. Conclusion

From this experiment we can see that the summing configuration provides a simple way to add two input voltage signals with negative fixed gain that can choose its value by changing R_2 Resistor.

And also we see one of the limitation of the summing and its Limited input voltage range, and the Frequency limit and slewing-rate limit.

9. Resources

All the Resources for this experiment including the pdf file and the simulation file and MATLAB scripts and pictures and etc..., are available on Github Repository just scan the next QR Code to get the link for that Repository.



Scan Here